

Master of Entrepreneurship in Technology and Innovation - 01

Session: Electronic Rapid Prototyping

Assignment N° 01:


Case study:

Lab Design


Presented by:

- Mr Mohammed Yacine DJEBBARI


Schematics:

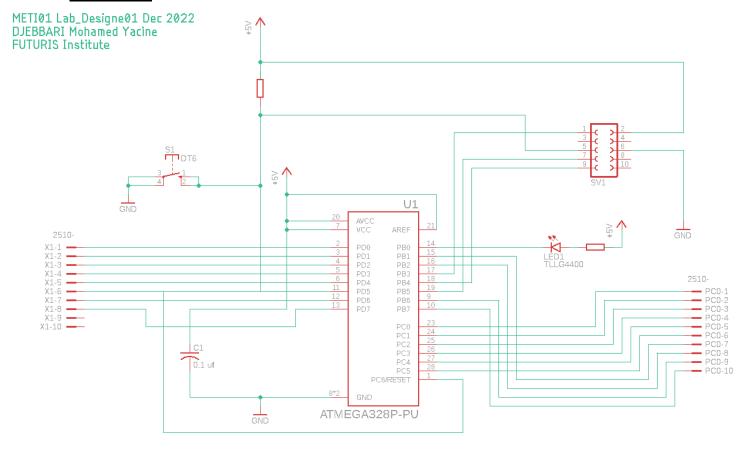

<u> PCB :</u>

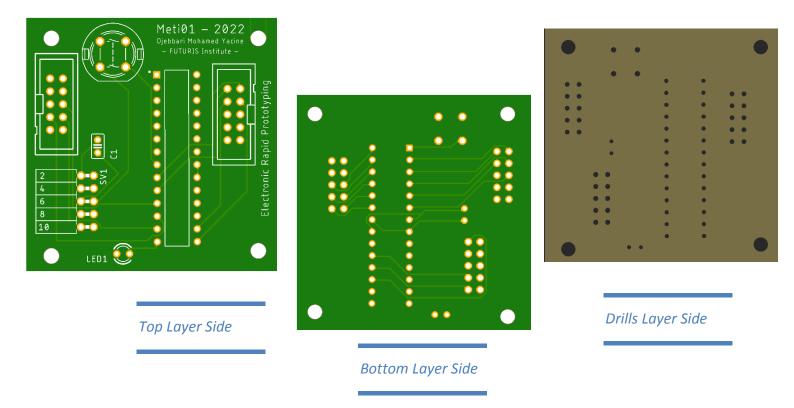

Board:

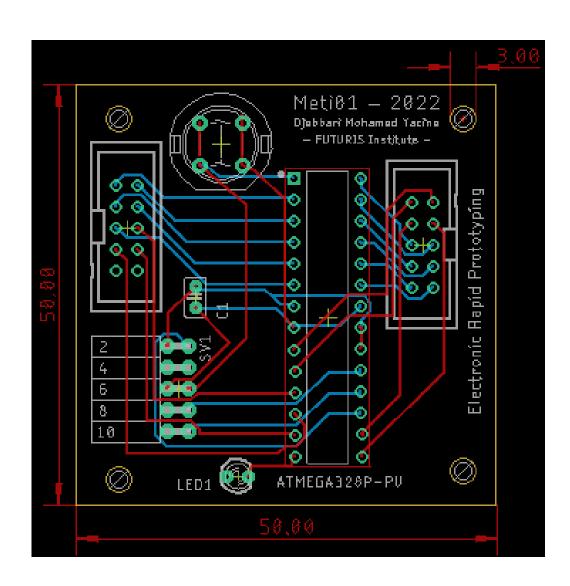

BOM file:

Qty	Value	Device	Package	Parts	Description
		FE05-2W	FE05-2W	SV1	FEMALE HEADER
	0.1 uf	C-US025-025X050	C025-025X050	C1	CAPACITOR, American symbol
	2510-	2510-	PAK100/2500-10	PC0, X1	3M (TM) Pak 100 4-Wall Header
	ATMEGA328P-PU	ATMEGA328P-PU	DIP794W46P254L2967H457Q28B	U1	ATmega Series 20 MHz 32 KB Flash 2 KB SRAM 8-Bit Microcontroller - DIP-28 Check availability
	DT6	DT6	DT6	S1	ITT SWITCH
	TLLG4400	TLLG4400	LED3MM	LED1	Low Current (2mA) LED 3 mm Tinted Diffused Package color GREEN